

# Differential R-to-V Converter

Monica S – 23B1243  
Rajpurohit Nikita – 24M1203

Guide: Prof. Maryam Shojaei Bhagini

October 12, 2025

**Reference:** M. Ahmad *et al.*, “An Auto-Calibrated Resistive Measurement System With Low Noise Instrumentation ASIC,” *IEEE Journal of Solid-State Circuits*, vol. 55, no. 11, pp. 3036–3050, Nov. 2020.

# Motivation

- Sensors such as **temperature sensors** and **strain gauges** change resistance with actuation.
- Most flexible wearable devices commonly use **resistive sensors**.
- Most processing circuits and ADCs work with **voltage signals**, hence a need for **R-to-V conversion**.
- A **differential R-to-V converter** minimizes mismatch effects.

# Half-Bridge over Wheatstone

- Using **Half-Bridge** instead of Wheatstone bridge for measurement:
  - Improved accuracy due to lesser mismatch effect.
  - Wider measurement range — Not limited by supply voltage.
  - Lower power consumption.

(Proposed solution : Auto-calibration enabled by programmable current source and INA gain)

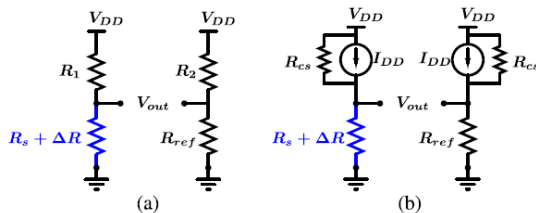


Figure: (a)Wheatstone bridge (b)Current-excited Half-Bridge

# Comparison of Wheatstone Bridge and Current Excitation Bridge

| Parameters                                                         | Wheatstone bridge                                                                               | Current excitation bridge                     |
|--------------------------------------------------------------------|-------------------------------------------------------------------------------------------------|-----------------------------------------------|
| Output voltage ( $V_{out}$ )                                       | $V_{DD} \cdot \frac{k \frac{\Delta R}{R_s}}{(1+k) \cdot \left(1+k+\frac{\Delta R}{R_s}\right)}$ | $I_{DD} \cdot \frac{\Delta R}{R_s} \cdot R_s$ |
| Sensitivity ( $\frac{\partial V_{out}}{\partial (\Delta R/R_s)}$ ) | $V_{DD} \cdot \frac{k}{(1+k+\frac{\Delta R}{R_s})^2}$                                           | $I_{DD} \cdot R_s$                            |
| PSRR ( $\frac{\partial V_{DD}}{\partial V_{out}}$ )                | $\frac{(1+k) \left(1+k+\frac{\Delta R}{R_s}\right)}{k \frac{\Delta R}{R_s}}$                    | $\frac{k}{\frac{\Delta R}{R_s}}$              |
| $k$                                                                | $\frac{R_1}{R_s} = \frac{R_2}{R_{ref}} = 1$                                                     | $\frac{R_{cs}}{R_s} > 1000$                   |
| Max Sensitivity at ( $\Delta R/R_s = 0$ )                          | $V_{DD}/4$                                                                                      | $I_{DD} \cdot R_s = V_{DD}/2$                 |
| PSRR at ( $\Delta R/R_s = 100\%$ )                                 | 15 dB                                                                                           | 60 dB                                         |

# Why Square Wave Current Excitation?

- **Current excitation** increases dynamic range.
- DC excitation suffers from thermoelectric effects.
- Generating pure sinusoidal excitation is power-hungry and requires complex circuitry.
- Square wave excitation:
  - Simpler to generate.
  - Contains harmonics handled by Differential Ratiometric Operation (DRO).

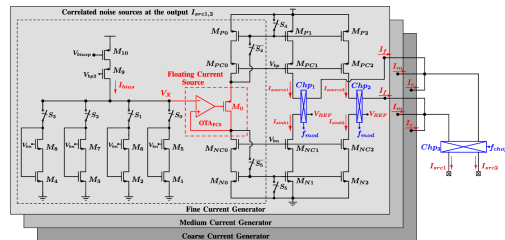


Fig. Square wave current generation

# Circuit Overview

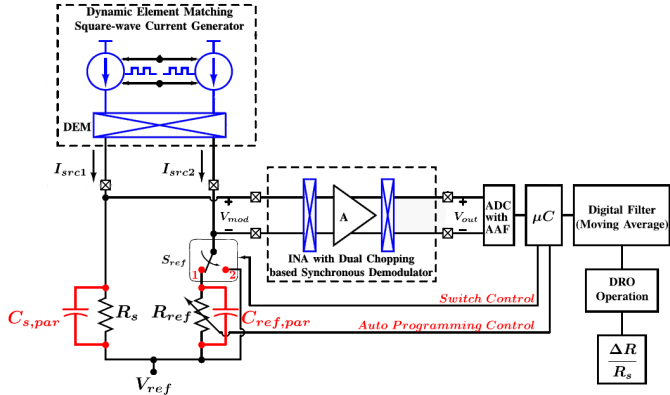


Figure: Proposed differential R-to-V converter system for  $\Delta R/R_s$  measurement.

# Circuit Overview

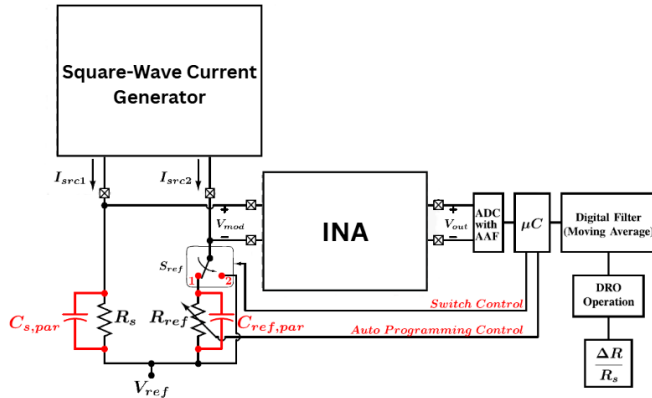


Figure: Proposed differential R-to-V converter system for  $\Delta R/R_s$  measurement.

# Instrumental Amplifier (INA)

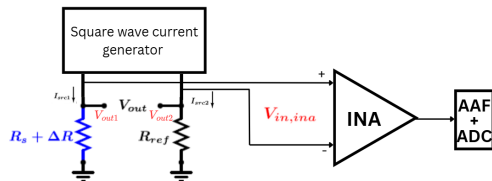


Fig: INA

$$I_{src1} = I_{src2}$$

$$R_s = R_{ref}$$

$$V_{out1} = I_s (R_s + \Delta R_s)$$

$$V_{out2} = I_s R_s$$


$$V_{out} = V_{out1} - V_{out2} = I_s \Delta R_s$$

- Provides high Common Mode Rejection Ratio (CMRR).


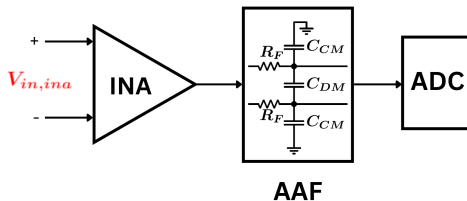
# Anti-Aliasing Filter

- Square waves contain odd harmonics of the fundamental frequency.
- Without filtering, harmonics alias into the signal band, leading to distortion.
- The AAF ensures accurate ADC sampling and signal reconstruction.




*Filter response showing attenuation of higher harmonics.*

# Differential Ratiometric Operation (DRO)

## Phase 1: Maximizing sensitivity

$$V_{out} = I_s \frac{\Delta R_s * R_s}{R_s}$$

$$S = I_s * R_s$$

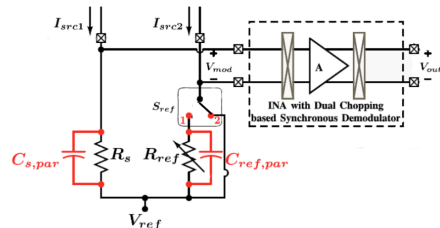


## Phase 2: Baseline resistance measurement

$$V_{out|phase\ 2} = I_{src}(t) \times R_s \times A \times V_{mod}(t)$$


$$I_{src}(t) = \frac{4I}{\pi} \sum_{n=1}^{\infty} \frac{1}{2n-1} \sin((2n-1)\omega_0 t)$$
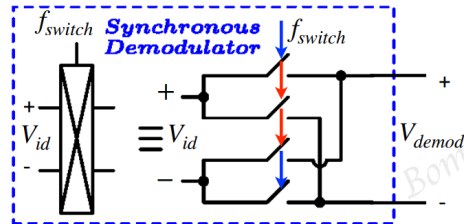
$$V_{mod}(t) = \frac{1}{\pi} \sum_{n=1}^{\infty} \frac{1}{2n-1} \sin((2n-1)\omega_0 t)$$



# Differential Ratiometric Operation (DRO)
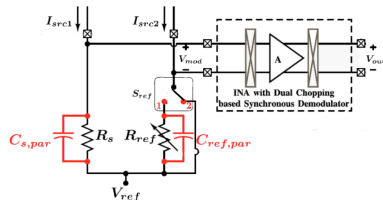
## Phase 2: Baseline resistance measurement



$$V_{out|phase\ 2} = \left(\frac{4}{\pi}\right)^2 I R_s A \sum_{n=1}^{\infty} \frac{\sin^2((2n-1)\omega_0 t)}{(2n-1)^2}$$


$$= \left(\frac{4}{\pi}\right)^2 I R_s A \cdot \frac{1}{2} \sum_{n=1}^{\infty} \left( \frac{1}{(2n-1)^2} - \frac{2 \cos(2(2n-1)\omega_0 t)}{(2n-1)^2} \right)$$

Oscillatory part is removed by Moving filter

$$V_{out|phase\ 2} = \left(\frac{4}{\pi}\right)^2 I \times A \times R_s \times D$$

$$\text{where } D = \sum_{n=1}^{\infty} \frac{1}{2} \cdot \frac{1}{(2n-1)^2}$$
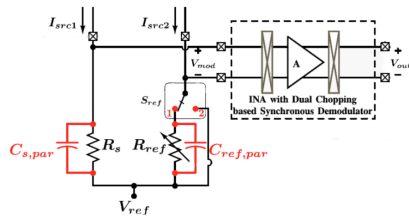
# Differential Ratiometric Operation (DRO)



## Phase 3: Mismatch calibration

In phase 3, ideally  $V_{out}$  should be zero, as  $R_{ref}$  is adjusted to  $R_s$

$$V_{out|phase\ 3} = \left(\frac{4}{\pi}\right)^2 A[I\delta R + \delta I(R_s - \delta R)]D$$

where;  $R_s - R_{ref} = \delta R$

$$I_{src1} - I_{src2} = \delta I$$

## Phase 4: Final measurement

$$V_{out|phase\ 4} = \left(\frac{4}{\pi}\right)^2 A[I(\Delta R + \delta R) + \delta I(R_s - \delta R)]D$$

Final Output:

$$\frac{\Delta R_s}{R_s} = \frac{V_{out|phase\ 4} - V_{out|phase\ 3}}{V_{out|phase\ 2}}$$

# Effect of Parasitic Capacitance

$$V_{\text{out}} = \left(\frac{4}{\pi}\right)^2 AI \sum_{n=1}^{\infty} \frac{1}{2(2n-1)^2} (Z_s - Z_{\text{ref}})$$

Sensor branch:  $R_s \parallel C_{s,\text{par}}$

Reference branch:  $R_{\text{ref}} \parallel C_{\text{ref},\text{par}}$

$$Z_{\text{eq}}(j\omega) = \frac{R}{1+j\omega C}$$

$$Z_s(n) = \frac{R_s}{1+j(2n-1)\omega R_s C_{s,\text{par}}}$$

$$Z_{\text{ref}}(n) = \frac{R_{\text{ref}}}{1+j(2n-1)\omega R_{\text{ref}} C_{\text{ref},\text{par}}}$$

$$\omega_{\text{clk}} \ll \frac{1}{R_s C_{s,\text{par}}}, \quad \omega_{\text{clk}} \ll \frac{1}{R_{\text{ref}} C_{\text{ref},\text{par}}}$$

$$V_{\text{out}} \approx \left(\frac{4}{\pi}\right)^2 \frac{A \cdot I}{2} \sum_{n=1}^{\infty} \frac{1}{(2n-1)^2} (R_s - R_{\text{ref}})$$


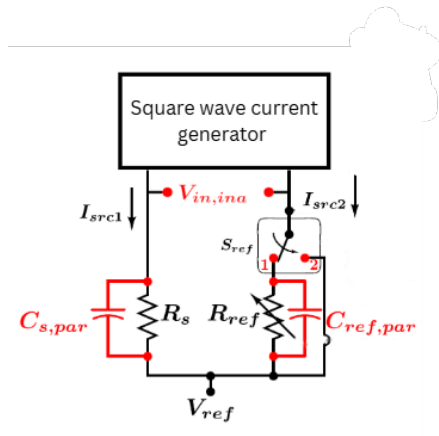
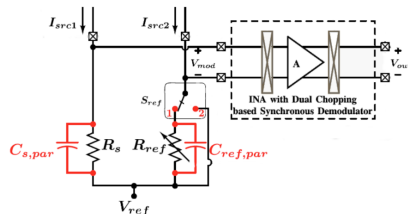


Fig.Effect of parasitic capacitance
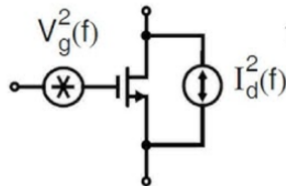
# Frequency Tradeoff

- Reducing excitation frequency decreases parasitic effects.
- However, lower frequencies increase MOSFET flicker noise.
- $V_g^2(f) = \frac{K}{WLC_{ox}f}$
- Thermal Noise:  $I_d^2(f) = 4kT(\frac{2}{3})g_m$



# Specifications

| Parameter                  | Value                                               |
|----------------------------|-----------------------------------------------------|
| Excitation Signal          | AC Current (Square)                                 |
| Technology Node            | 180nm                                               |
| Supply                     | 1.8V                                                |
| Base Resistor $R_s$        | 1k $\Omega$ – 500k $\Omega$                         |
| Excitation Current (Prog.) | 0.1 $\mu$ A – 44.4 $\mu$ A                          |
| CMRR of INA                | >110 dB                                             |
| Power                      | 33.3 $\mu$ W @ 100 nA<br>357 $\mu$ W @ 44.4 $\mu$ A |
| ADC resolution             | 15 bit                                              |

| Max $\Delta R/R$                                                 | Min $\Delta R/R$                                            |
|------------------------------------------------------------------|-------------------------------------------------------------|
| $\pm 135\%$ @ $R_s = 10 \text{ k}\Omega$ , $I = 4.4 \mu\text{A}$ | 26 ppm @ $R_s = 10 \text{ k}\Omega$ , $I = 4.4 \mu\text{A}$ |
| $\pm 120\%$ @ $R_s = 0.5 \text{ M}\Omega$ , $I = 100 \text{ nA}$ | 72 ppm @ $R_s = 0.5 \text{ M}\Omega$ , $I = 100 \text{ nA}$ |

# Any Questions?



# Comments

- Add required figure on every slide.
- Draw switch positions in figure.

According to the feedback received in presentation- 1, the slides are modified.